



# **Asynchronous & Synchronous Reset Design Techniques - Part Deux**

**Clifford E. Cummings**  
Sunburst Design, Inc.  
cliffc@sunburst-design.com  
www.sunburst-design.com

**Don Mills**  
LCDM Engineering  
mills@lcm-eng.com  
www.lcm-eng.com

**Steve Golson**  
Trilobyte Systems  
sgolson@trilobyte.com  
www.trilobyte.com

# Agenda

## "Resets Update & FAQ"

---



- Flip-flop coding styles
- Synchronous resets
- Asynchronous resets
- Design For Test (DFT) considerations
- Reset-buffer tree
  - Distributed synchronous reset flip-flops
  - Distributed asynchronous reset synchronizers
- Synthesis issues with reset nets
- Multi-clock resets

Reference slides  
only

- Problem: dissimilar flip-flops in the same always block

```


module badFFstyle (q2, d, clk, rst_n);
  output q2;
  input  d, clk, rst_n;
  reg    q2, q1;

  always @(posedge clk)
    if (!rst_n) q1 <= 1'b0;
    else begin
      q1 <= d;
      q2 <= q1;
    end
endmodule

```

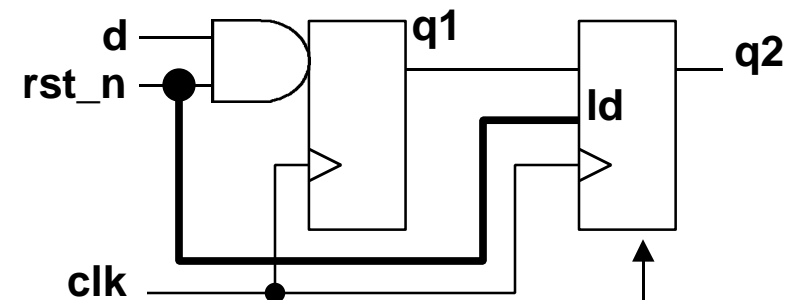q2 is only loaded  
if rst\_n is high

**BAD PARTITIONING Style  
creates EXTRA LOGIC**



rst\_n becomes a  
"load-data" signal

**VHDL model included in the paper**

- Solution: put dissimilar flip-flops in separate always blocks

```

module goodFFstyle (q2, d, clk, rst_n);
  output q2;
  input  d, clk, rst_n;
  reg    q2, q1;

  always @(posedge clk)
    if (!rst_n) q1 <= 1'b0;
    else       q1 <= d;


  always @(posedge clk)
    q2 <= q1;
endmodule

```

q2 is loaded on every  
posedge clk

Note: To model sequential logic  
use nonblocking assignments

Good partitioning -  
no extra logic

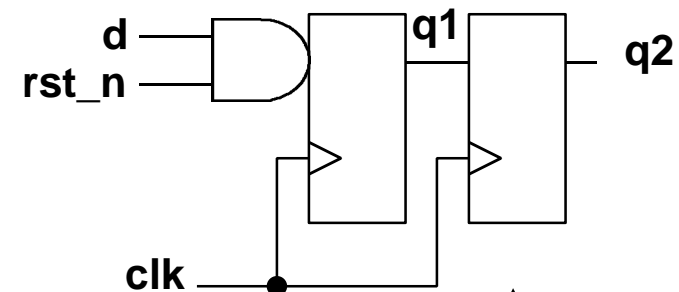

No reset on the  
follower flip-flop

VHDL model included in the paper

- Synchronous reset: `rst_n` is not in the sensitivity list

```

module ctr8sr ( q, co, d, ld, rst_n, clk);
  output [7:0] q;
  output      co;
  input  [7:0] d;
  input      ld, rst_n, clk;
  reg      [7:0] q;
  reg      co;

  always @(posedge clk)
    if      (!rst_n) {co,q} <= 9'b0;      // sync reset
    else if (ld)    {co,q} <= d;          // sync load
    else          {co,q} <= q + 1'b1;    // sync increment
endmodule

```

`rst_n` not in the  
sensitivity list


VHDL model included in the paper

VHDL versions would have required too  
many slides to show the same models ...

... or a microscopic font

# Synchronous Resets

## Synthesis Results #1

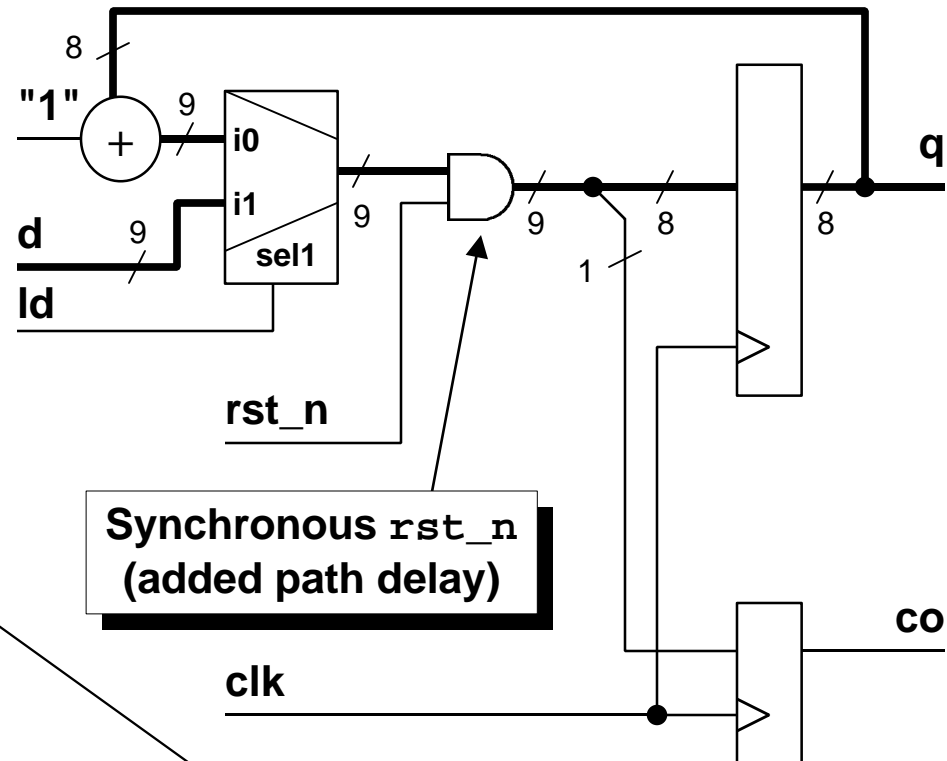

**clk is in the sensitivity list**

**Only clk can trigger the always block**

**Only clk can cause the outputs to change**

**rst\_n & ld are not in the sensitivity list (synchronous to clk)**

**Synchronous rst\_n (added path delay)**


```
always @(posedge clk)
  if      (!rst_n) {co,q} <= 9'b0;
  else if (ld)    {co,q} <= d;
  else          {co,q} <= q + 1'b1;
```

# Synchronous Resets
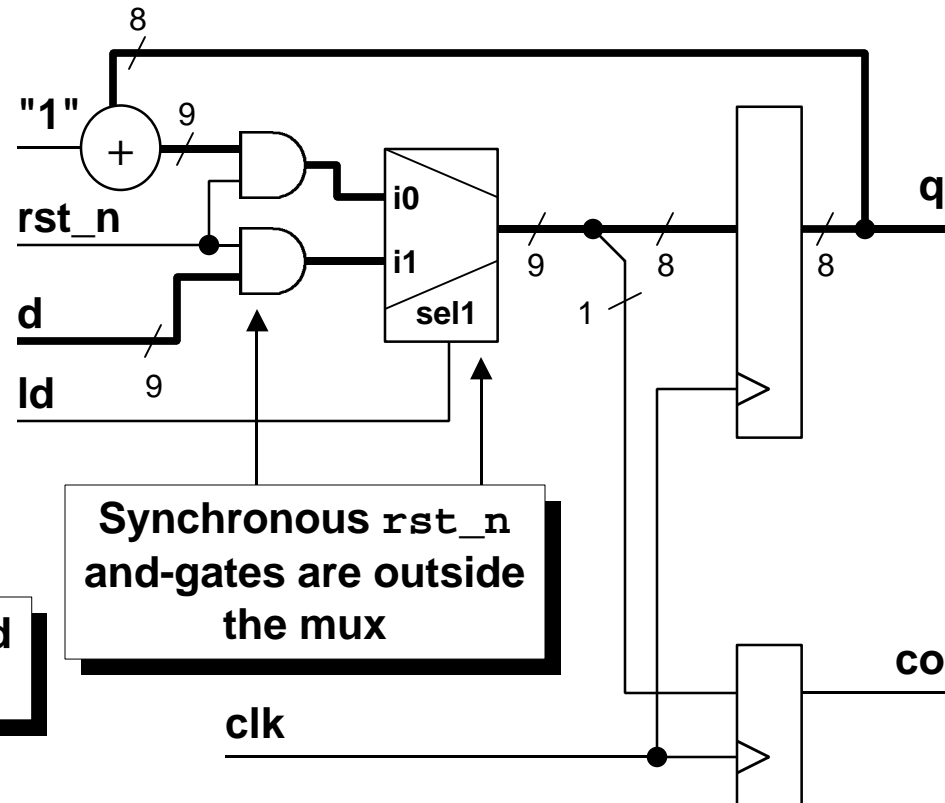
## Synthesis Results #2



**Synthesis tools could locate  
synchronous resets signals poorly**



**Synchronous `rst_n`  
and-gates are outside  
the mux**

**Add this directive to avoid badly placed  
synchronous reset signals**

```
// synopsys sync_set_reset "rst_n"
always @(posedge clk)
  if      (!rst_n) {co,q} <= 9'b0;
  else if (ld)     {co,q} <= d;
  else           {co,q} <= q + 1'b1;
```

- Asynchronous reset: rst\_n is in the sensitivity list

```

module ctr8ar ( q, co, d, ld, rst_n, clk);
  output [7:0] q;
  output      co;
  input  [7:0] d;
  input      ld, rst_n, clk;
  reg  [7:0] q;
  reg      co;

  always @(posedge clk or negedge rst_n)
    if      (!rst_n) {co,q} <= 9'b0;      // async reset
    else if (ld)    {co,q} <= d;          // sync load
    else          {co,q} <= q + 1'b1;    // sync increment
endmodule


```

rst\_n is in the  
sensitivity list

VHDL model included in the paper



# Synthesizing Asynchronous Resets

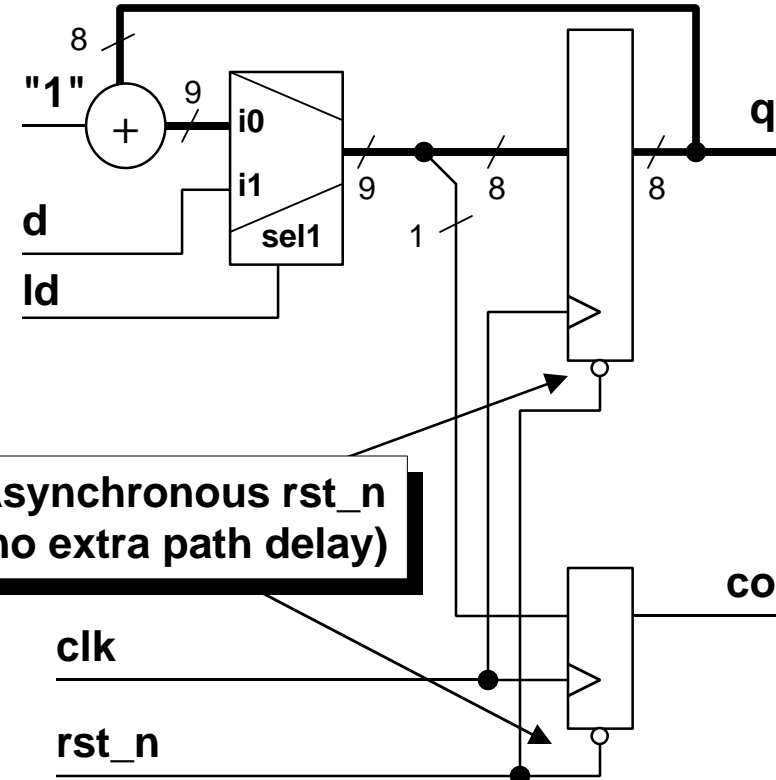

Only *clk* or *rst\_n* can cause the outputs to change

*clk* or *rst\_n* can trigger the always block

```
always @(posedge clk or negedge rst_n)
  if      (!rst_n) {co,q} <= 9'b0;
  else if (ld)    {co,q} <= d;
  else          {co,q} <= q + 1'b1;
```

Asynchronous *rst\_n* (no extra path delay)

asynchronous *rst\_n*, in the sensitivity list

synchronous *ld* not in the sensitivity list

# Synchronous Resets

## Advantages & Disadvantages

---



- Advantages

- Easier to work with cycle based simulators (according to the RMM)
- Typically recommended for DFT design
- Glitch filtering from reset combinational logic (to make up for poor design practices)
- Glitch filtering if reset is in a mission-critical application


- Disadvantages

- May not be able to come out of Unknown-X during simulation
- May add delay to data path
- Power-up resetting of a tri-state bus


← ... but there is  
a solution!

# Tri-State Enable Drivers

**Easy with an asynchronous resets**

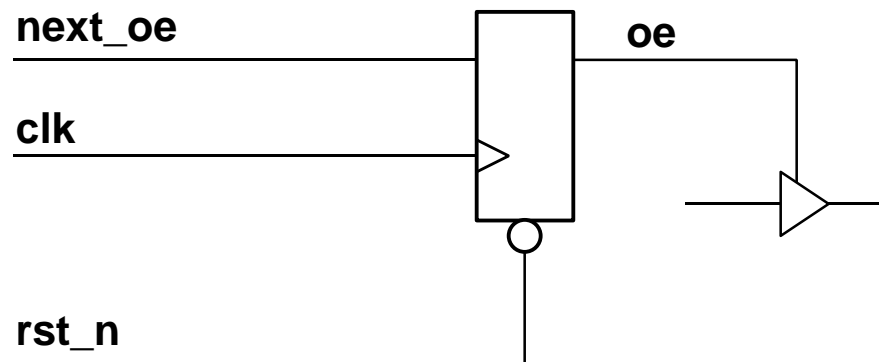

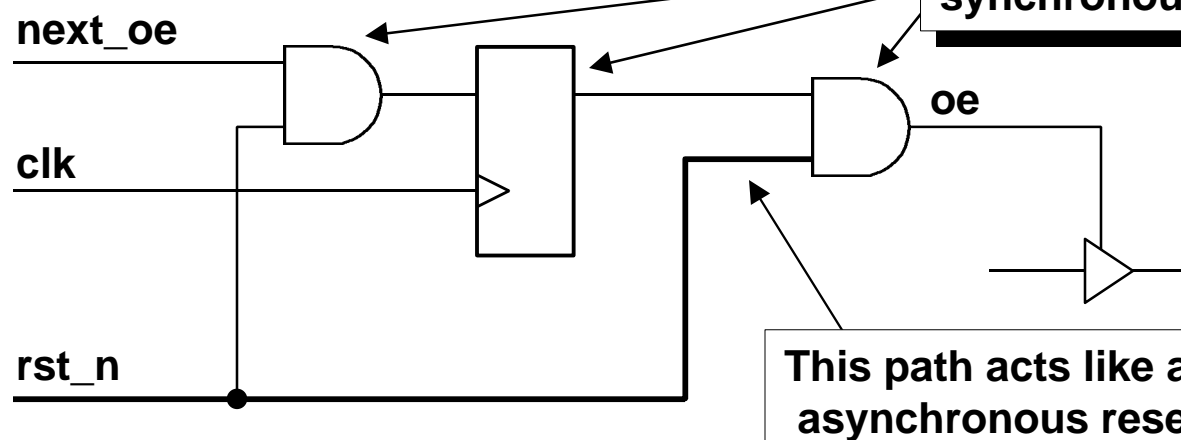**Not difficult with synchronous resets**



# Asynchronous Resets

## Advantages & Disadvantages

---



- Advantages

- Reset is immediate
- No problem related to Unknown-X-propagation in design simulation
- Does not interfere or add extra delay to the data path
- Very easy to implement on the front end

- Disadvantages


- Asynchronous signal - can go metastable on release
- Noisy reset line could cause unwanted resets
- DFT requires extra steps
- Requires reset buffer tree manipulation

**... but there is  
a solution!**

**... but this can  
be filtered**

**... but this can be  
fixed**

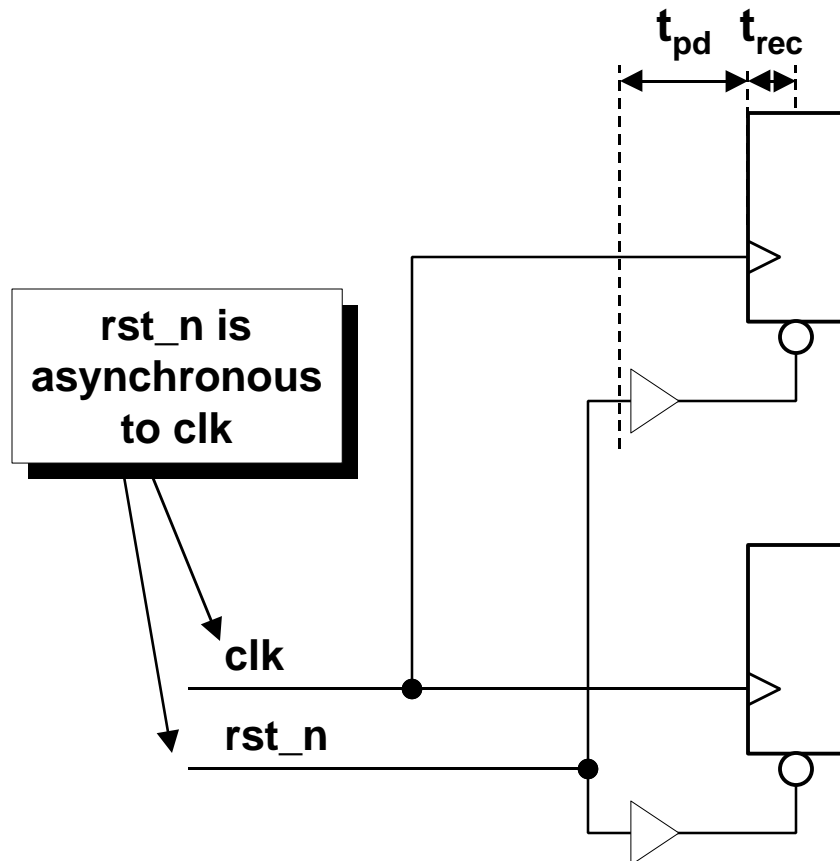- Problem: Asynchronous reset removal
  - Will reset removal meet recovery time specification?




Potential problem: flip-flop could go metastable on reset-release if reset removal violates clock set/hold time
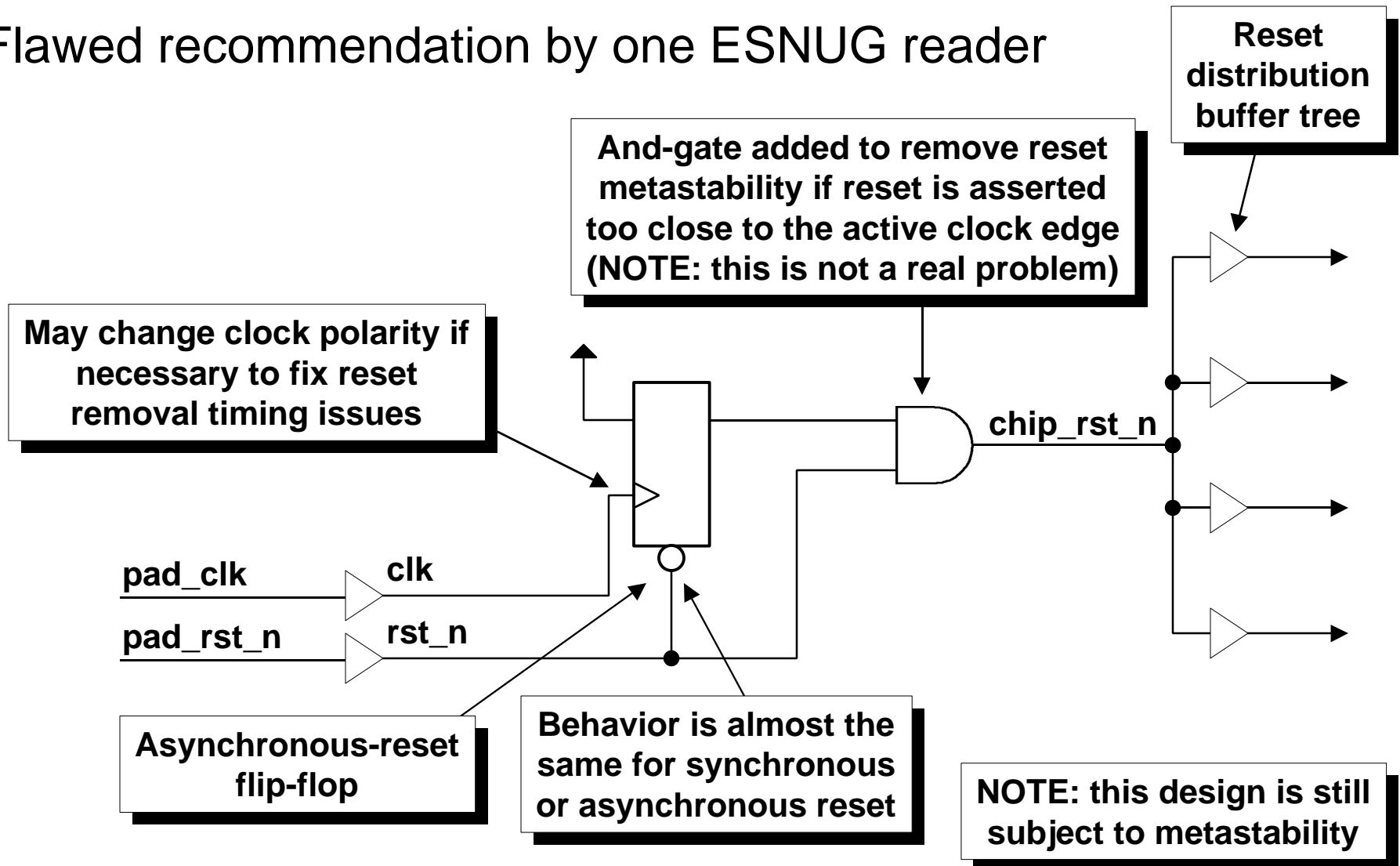
# Flawed Reset Synchronizer

(ESNUG 409 Item 11)



- Flawed recommendation by one ESNUG reader



# Flawed Reset RTL Thinking

(ESNUG 409 - Also Item 11)



- Flawed RTL coding thoughts by another ESNUG reader

**"One reason not to use asynchronous resets is that Verilog cannot model them without a race condition. Typical async reset flop:**

```
always @ (posedge ck or negedge rst) begin
    if (!rst) q <= 0;
    else      q <= d;
end
```

**A real hardware reset recovery violation!**

**"What happens when rst is DEasserted at the same time as ck is asserted?  
Either ck goes high first, and rst is still low, so q gets zero.  
Or rst goes high first, and when ck fires, q gets d.**

**Uh-oh. Do you get your new d or not?"**

**This is not a Verilog race condition,  
this is a hardware race condition!**

**Even with VHDL delta-times  
this same "race" condition exists**

# Flawed Reset RTL Thinking

(ESNUG 409 - Also Item 11 - continued)



- Upon further investigation, the real issue was poor testbench practices

```
always @ (posedge ck or negedge rst) begin
  if (!rst) q <= 0;
  else      q <= d;
end
```

**Users remove reset on the  
posedge clk in testbenches  
(What?? No Way!!)**

**Non-deterministic behavior between RTL and  
gates (and between different vendors)**


**Users blame EDA vendors when RTL  
differs from gates simulations**

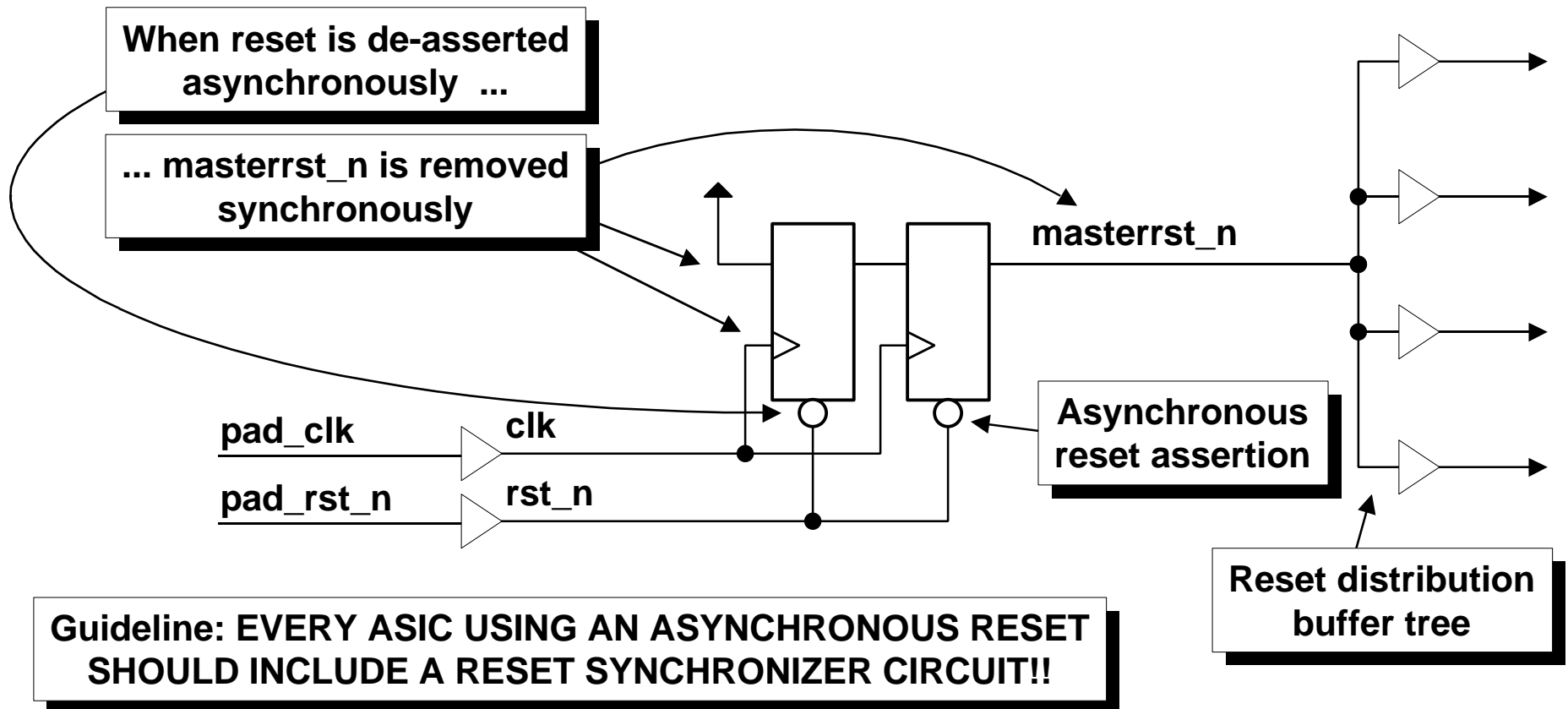**EDA vendors cannot fix real hardware race conditions!**

**Don't be a stupid user! Don't try removing reset on a posedge clk in the testbench!  
It doesn't work in simulations because it doesn't work in real hardware!!**



- Advantage: Asynchronous reset assertion
- Advantage: Synchronous reset removal




# Synchronous Reset Removal Solution




- Advantage: Synchronous reset removal
  - Predictable reset removal to meet recovery time specification!

 **Guideline: EVERY ASIC USING AN ASYNCHRONOUS RESET SHOULD INCLUDE A RESET SYNCHRONIZER CIRCUIT!!**



# Reset Synchronizer

Verilog RTL Code

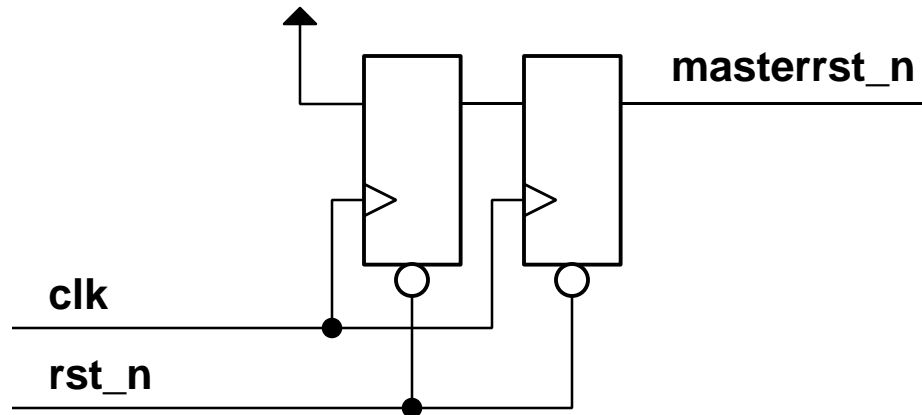

**Guideline: EVERY ASIC USING AN ASYNCHRONOUS RESET SHOULD INCLUDE A RESET SYNCHRONIZER CIRCUIT!!**

```
module reset_synchronizer (masterrst_n, clk, rst_n);
    output masterrst_n;
    input  clk, rst_n;
    reg    rst_n, rff1;

    always @(posedge clk or negedge rst_n)
        if (!rst_n) {masterrst_n,rff1} <= 2'b0;
        else        {masterrst_n,rff1} <= {rff1,1'b1};
endmodule
```

**Asynchronous  
reset assertion  
(on negedge rst\_n)**

**Synchronous  
reset removal  
(on posedge clk)**


**Concatenation makes for efficient  
coding of the reset synchronizer**



# Reset Removal Metastability??

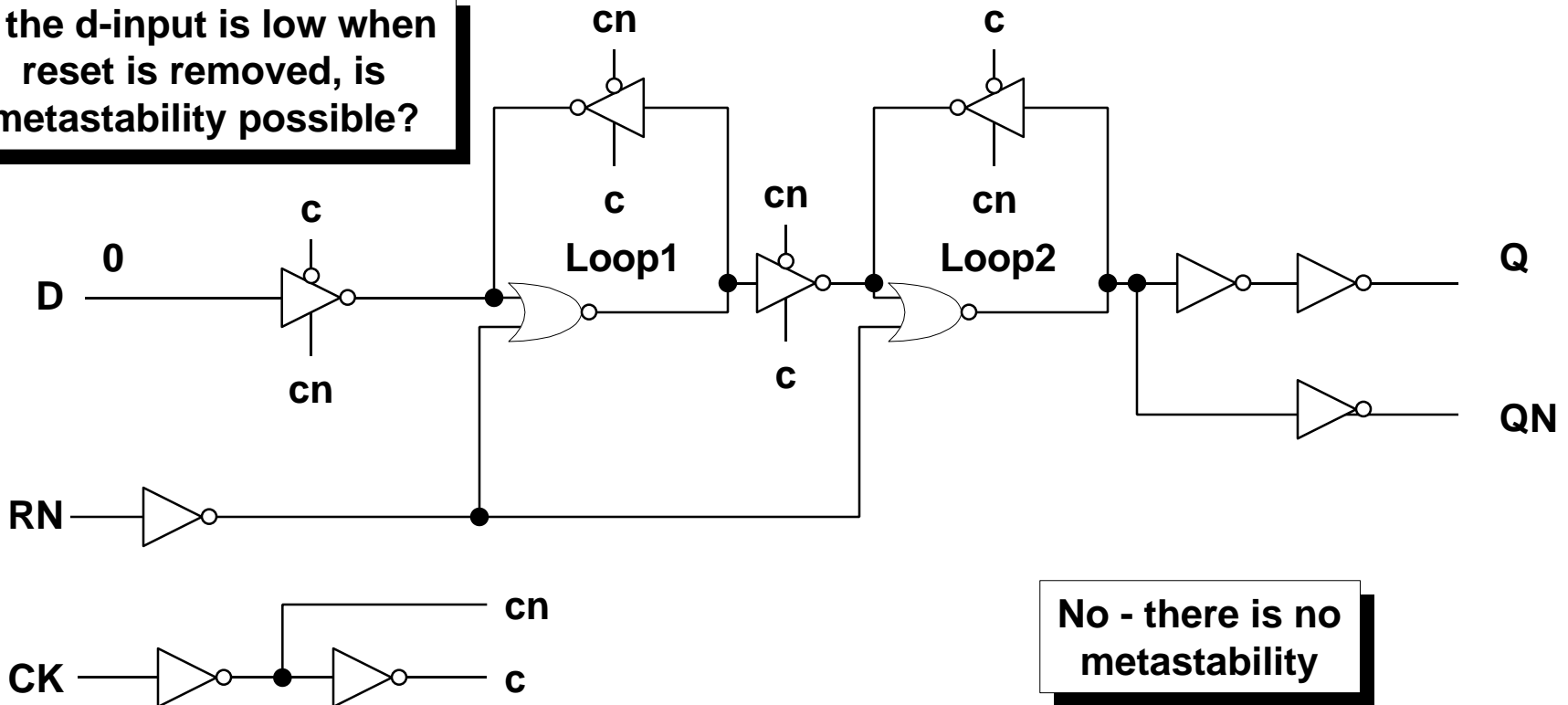- Example flip-flop implementation

If the d-input is low when reset is removed, is metastability possible?




No - there is no metastability
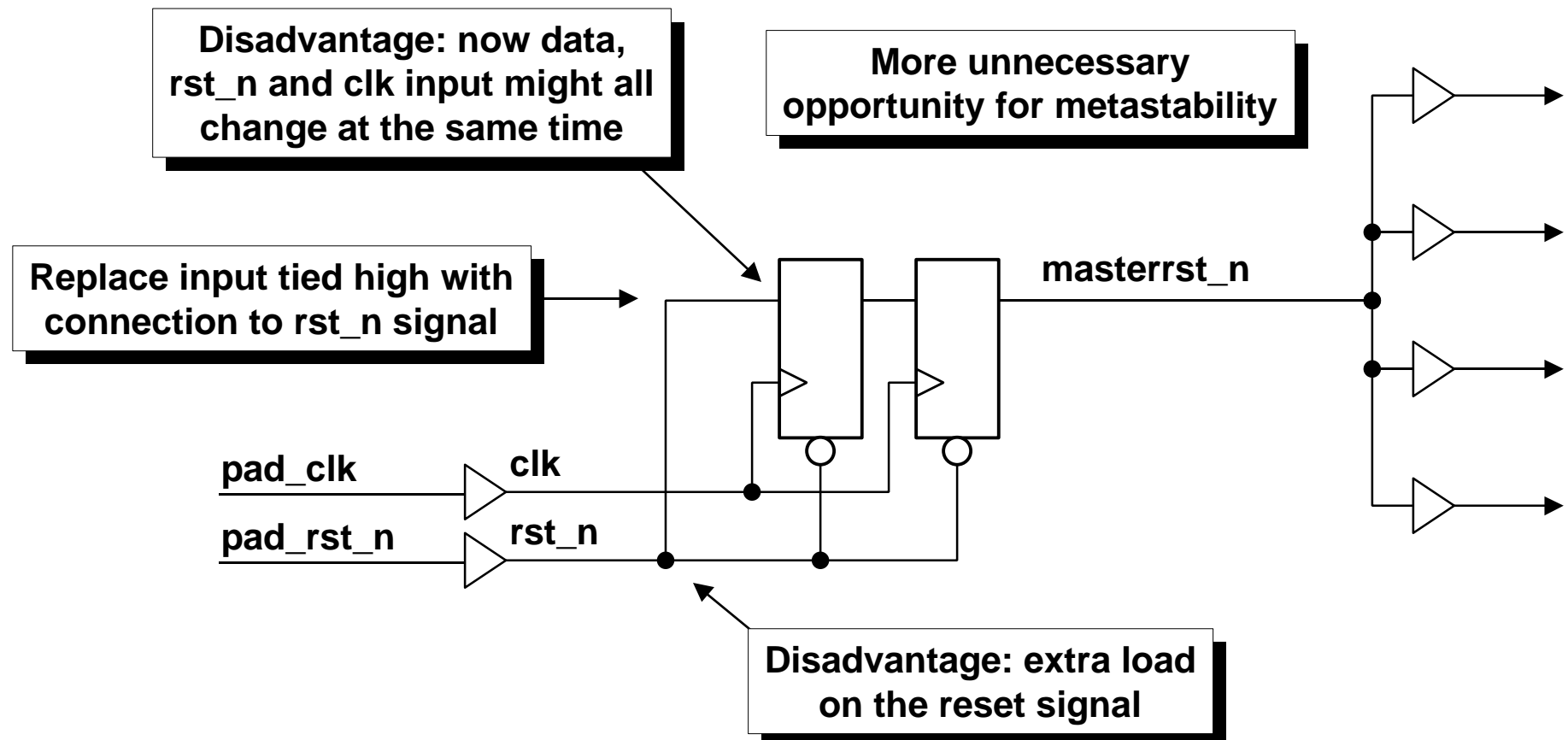
# Different Reset Synchronizer

(ESNUG 409 - Also Item 11)



- Tie the synchronizer data input to the reset input signal



# Synopsys Reset Switches



## Important reset-net switches

### Standard switches for reset nets

`set_drive 0`

`set_dont_touch_network`

To set 0-resistance on a reset net  
(ESNUG #355, Item 2 &  
ESNUG #356, Item 4)

`set_resistance 0`

Apply 0-resistance to the reset  
port with a custom wireload  
model in which resistance=0

`set_wire_load -port_list reset`

**Pre-Synopsys 2001.08 - do both**

`set_ideal_net`


`set_false_path & set_disable_timing`

Added to v2001.08: to create  
ideal nets and force no timing  
updates, no delay optimization,  
and no DRC fixing - *use with*  
*set\_false\_path & set\_disable\_timing*  
(SolvNet, Synthesis-780,  
Physical\_Synthesis-231,  
Synthesis-482109)

**Synopsys 2001.08 - `set_ideal_net`  
removes transition time propagation**

**Coming to Synopsys 2002.05 - set ideal "network"**


# Clock & Reset Loading

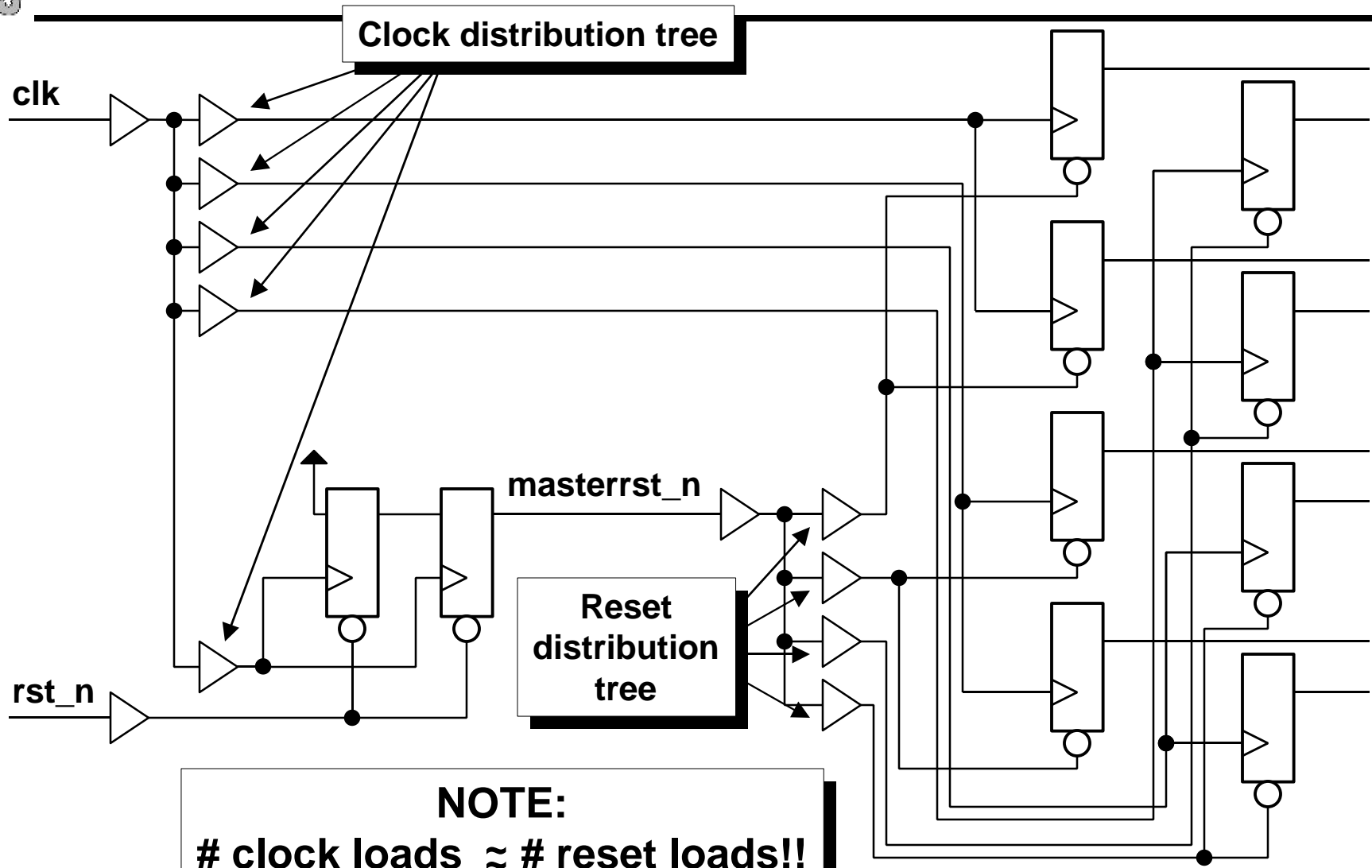




# Reset Buffer Tree

Driven from a Leaf-Driver Clock

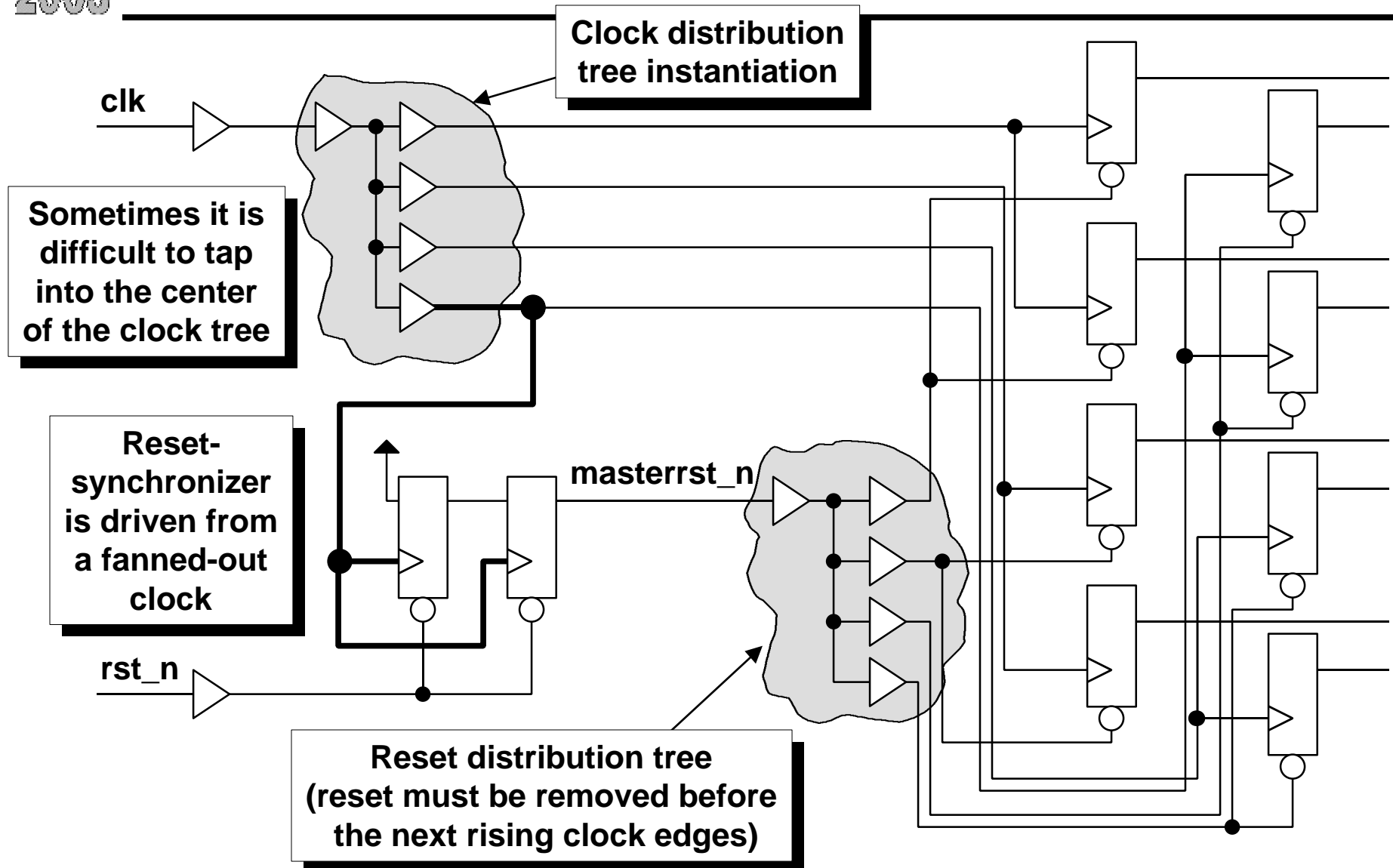

# Reset Buffer Tree

Driven from a Source-Driver Clock

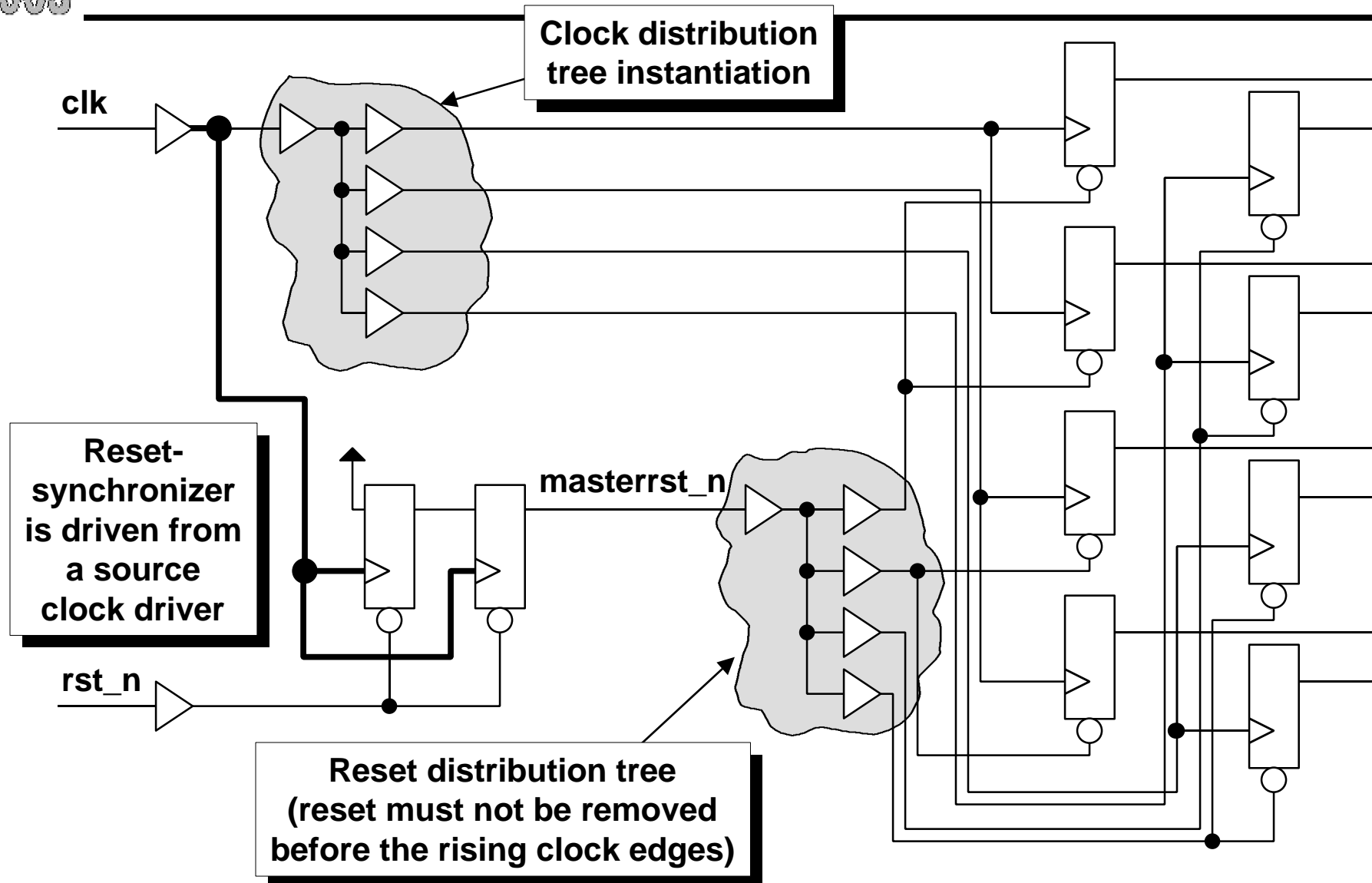

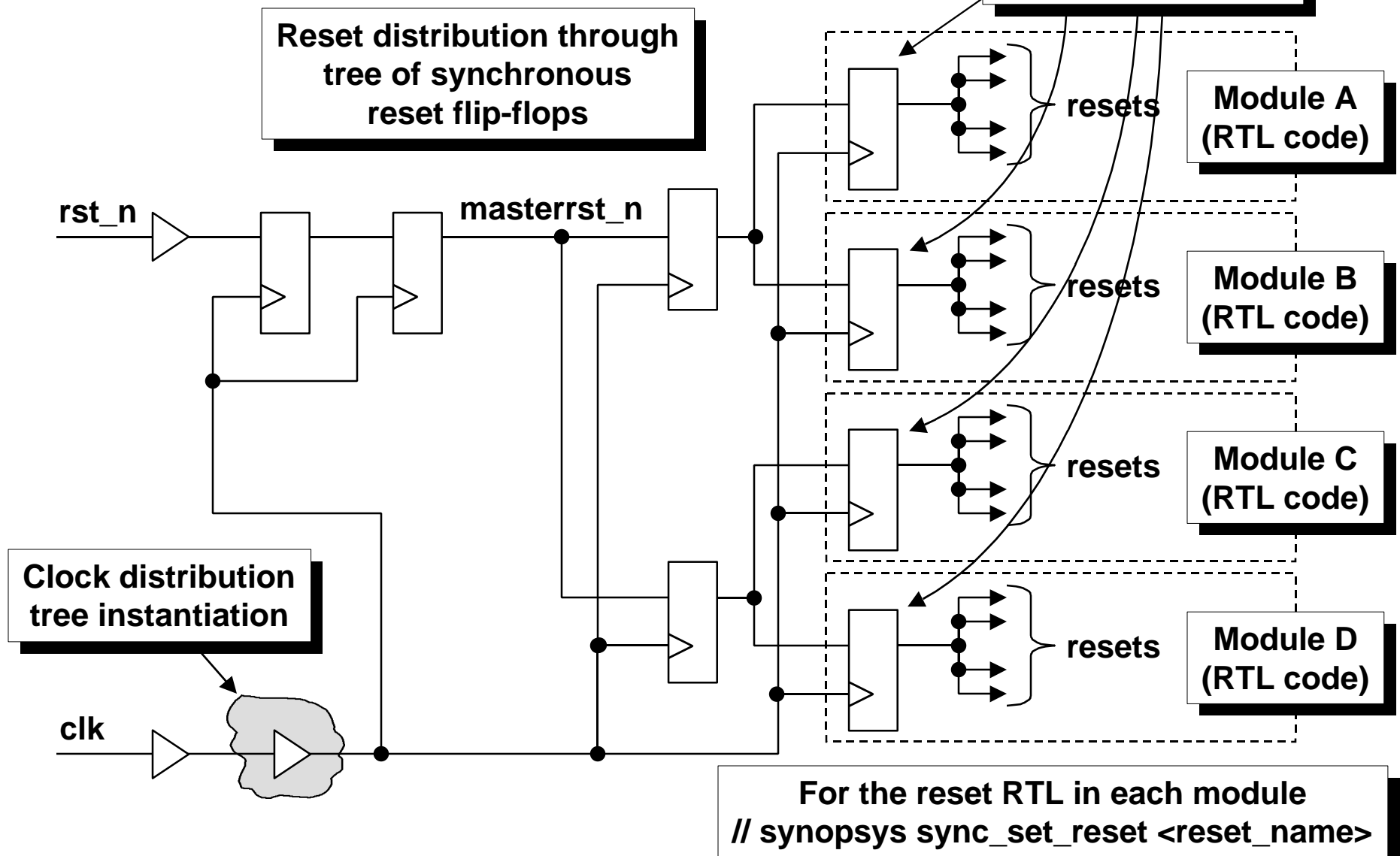
# Synchronous Reset Distribution using Flip-Flops



**Input reset flip-flop  
in each module**


**Reset distribution through  
tree of synchronous  
reset flip-flops**


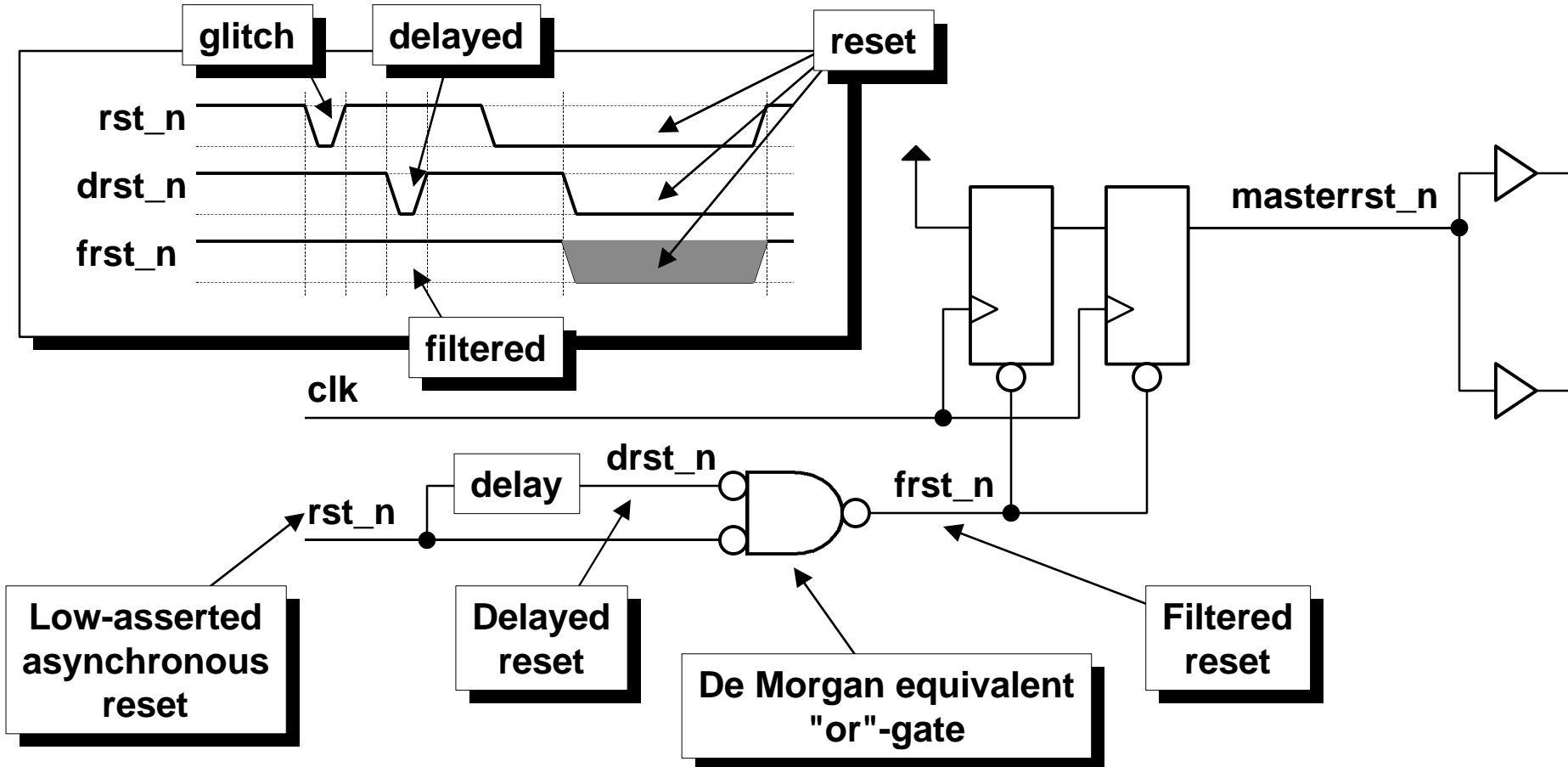
# Asynchronous Reset Glitch Filtering



- Glitches on the rst\_n input might cause stray resets
- Solution: glitch-filter on the rst\_n input



# Asynchronous Reset & DFT

---

- The process of applying the ATPG vectors to create a test is based on:
  - scanning a known state into all the flip-flops in the chip
  - switching the flip-flops from scan shift mode, to functional data input mode
  - applying one functional clock
  - switching the flip-flops back to scan shift mode to scan out the result of the one functional clock while scanning in the next test vector
  - During the above process, the designer must insure that under NO CONDITIONS, an asynchronous set/reset can occur and thus corrupt the input vectors

**The asynchronous reset must be held in the inactive state during the entire test**

**What about coverage to the portion of the chip controlled by the reset?**

# Asynchronous Reset & DFT

---

- Can I use an asynchronous reset with Design For Test (DFT) strategies?
  - scan in all ones into the scan chain
  - issue and release the asynchronous reset
  - scan out the result and scan in all zeros
  - issue and release the reset
  - scan out the result
  - set the reset input to the non reset state and then apply the ATPG generated vectors


**This will test for the reset line attached to either the asynchronous set or reset of a flip-flop**

# Multiple Clock Domains
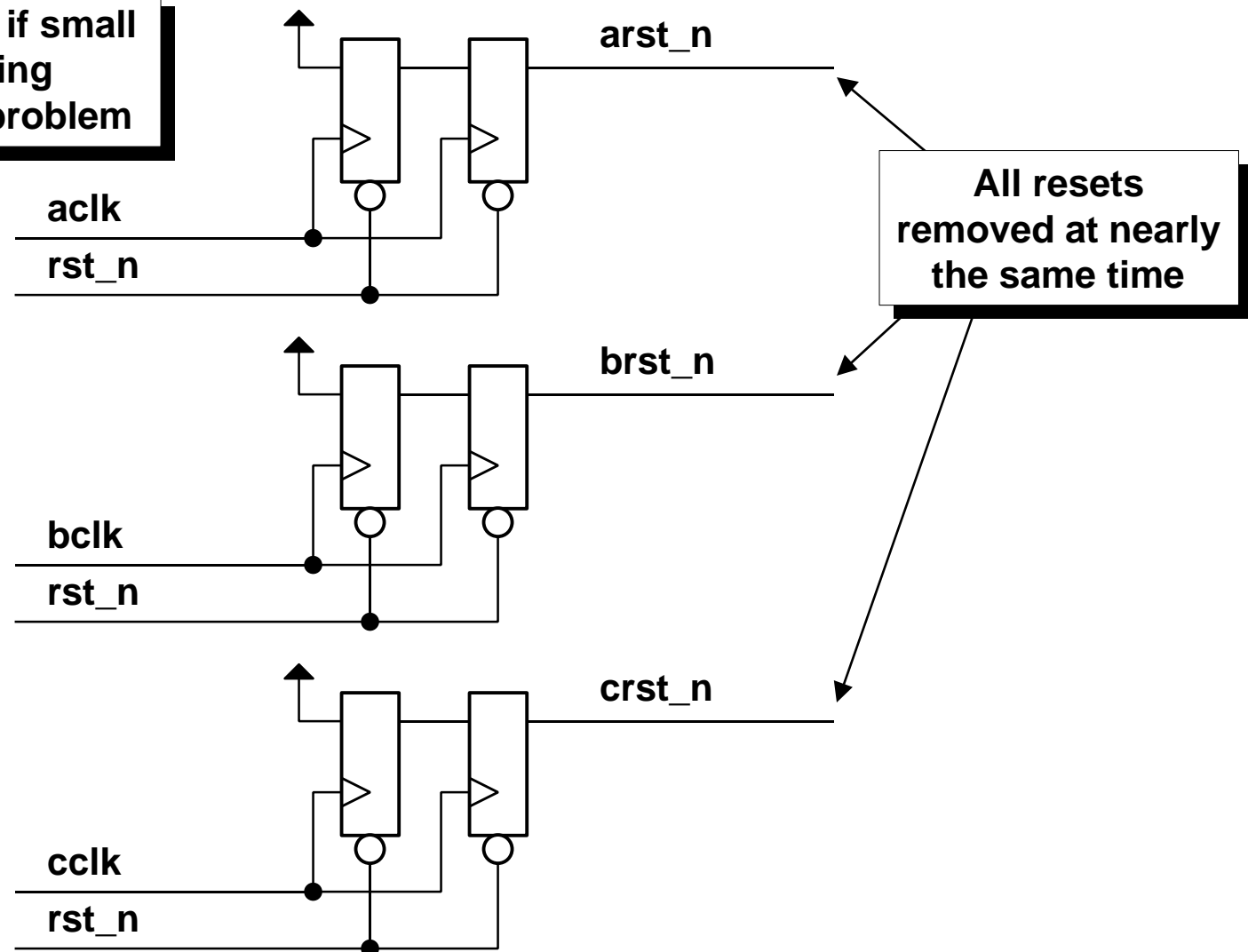
## Non-Synchronized Reset Removal




This technique works if small reset removal timing differences are not a problem



# Multiple Clock Domains

## Synchronized Reset Removal

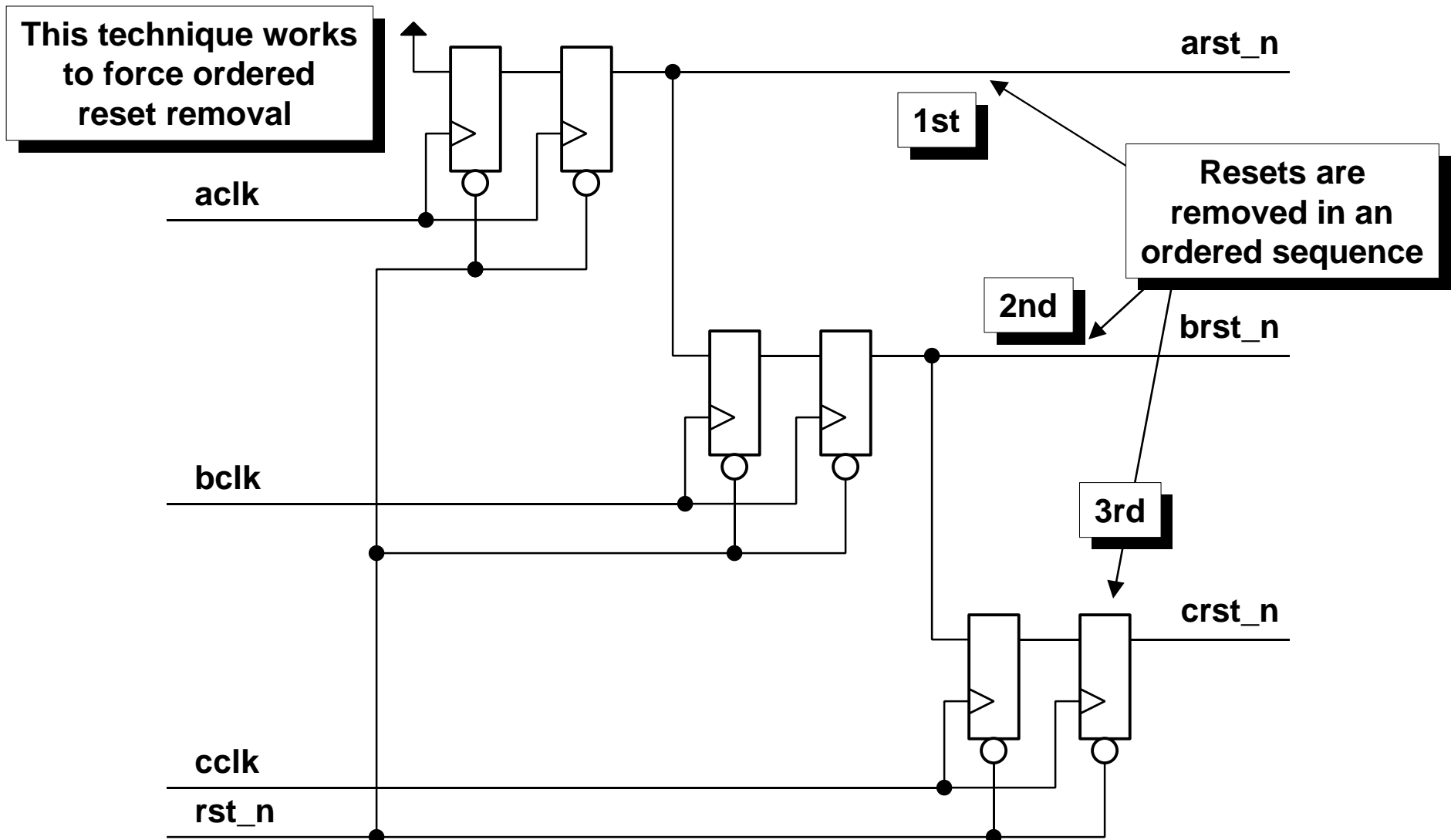



- Synchronous resets:
  - Add "`synopsys sync_set_reset`" directive to optimize synchronous reset layout (and minimize X-state simulation problems)
  - Easiest solution for doing Static Timing Analysis (STA)
  - Easiest solution when working with DFT
- Asynchronous resets and the "Reset Synchronizer":
  - Offers the advantages of asynchronous resets
  - Offers the advantages of synchronous reset removal
  - Still works well with DFT techniques
  - Reset path is not as easily checked using STA
- Know the limitations of each reset strategy
  - If you do it wrong it is gonna hurt!